



The Basic Logic Operations

- Each logic operation can be represented using:
 - a **schematic symbol (gate)**,
 - a **logic expression**,
 - or a **truth table**.

